

## EXPERIMENT- 5

**Objective:** To study the RC Phase Shift Oscillator.


**Resources Required:** Trainer kit of RC Phase Shift Oscillator.

### **Theory :**

RC phase-shift oscillators use resistor-capacitor (RC) network (Figure 1) to provide the phase-shift required by the feedback signal. They have excellent frequency stability and can yield a pure sine wave for a wide range of loads. Ideally a simple RC network is expected to have an output which leads the input by  $90^\circ$ . However, in reality, the phase-difference will be less than this as the capacitor used in the circuit cannot be ideal. Mathematically the phase angle of the RC network is expressed as  $\varphi = \tan^{-1}(X_c/R)$ .

Where,  $X_C = 1/(2\pi fC)$  is the reactance of the capacitor C and R is the resistor. In oscillators, these kind of RC phase-shift networks, each offering a definite phase-shift can be cascaded so as to satisfy the phase-shift condition led by the Barkhausen Criterion. Here the collector resistor  $R_C$  limits the collector current of the transistor, resistors  $R_1$  and  $R$  (nearest to the transistor) form the voltage divider network while the emitter resistor  $R_E$  improves the stability. Next, the capacitors  $C_E$  and  $C_0$  are the emitter by-pass capacitor and the output DC decoupling capacitor, respectively. Further, the circuit also shows three RC networks employed in the feedback path.

### **Circuit Diagram :**

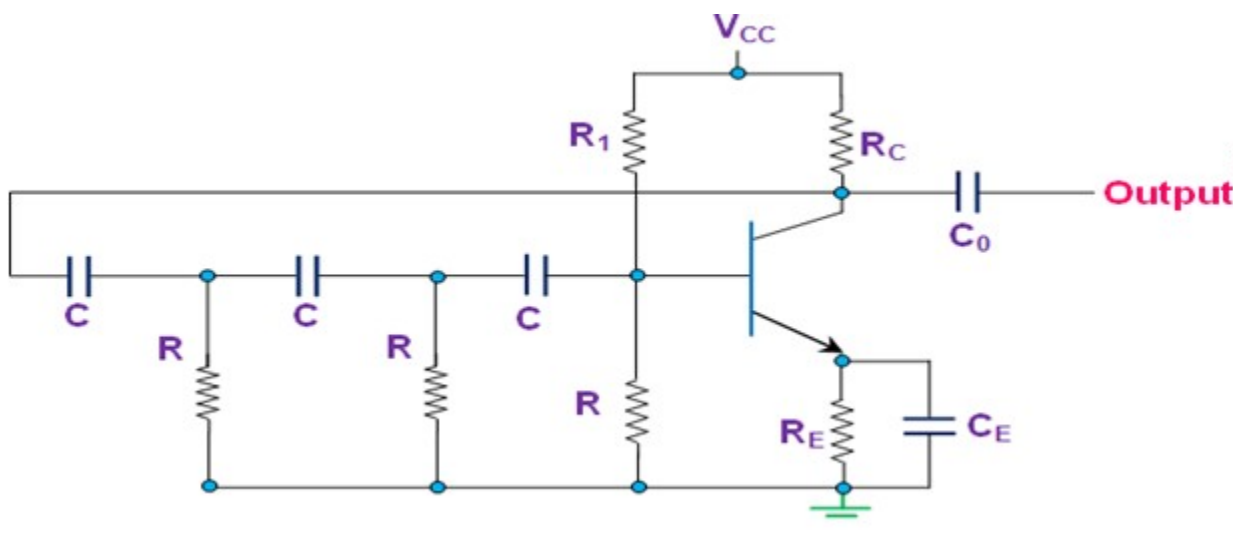

**Fig: RC Phase Shift Oscillator**

**Procedure:-**

1. We should take all the components for this experiment.
2. Make the connection as per circuit diagram.
3. Switch ON the kit using ON/OFF toggle switch
4. The input signal is applied with the function generator
5. Then observe the wave form
6. Calculate the frequency using formulae  $f = 1/2\pi RC$

**RESULT:**

Frequency of oscillation of wien bridge oscillator is calculated