

## EXPERIMENT-3

**Objective:** To design and simulate full adder using VHDL.

**Resources Required:**

Hardware Requirement: Computer

Software Requirement: XILINX 8.2 Software

**Theory:**

Full adder is the adder which adds three inputs and produces two outputs. The first two inputs are **a** and **b** and the third input is an input carry as **c**. The output carry is designated as **cy** and the normal output is designated as **s** which is SUM.

**Truth Table:**

INPUTS			OUTPUTS	
a	b	c	s	cy
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Boolean Expression**

$$s = (a \text{ xor } b) \text{ xor } c;$$
$$cy = (a \text{ and } b) \text{ or } (b \text{ and } c) \text{ or } (c \text{ and } a);$$


**VHDL Code:**

```
Dataflow Modelling
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
    --Entity Declarations
entity fulladder is
port(a,b,c: in std_logic;
      s,cy: out std_logic);
end fulladder;
```

```
architecture dataflow of fulladder is
begin
s<= (a xor b)xor c;
cy<= (a and b) or (b and c) or (c and a);
end dataflow;
```

**Output:**

**RTL Schematic**

 

**Results:** VHDL codes of full adder is simulated & synthesized