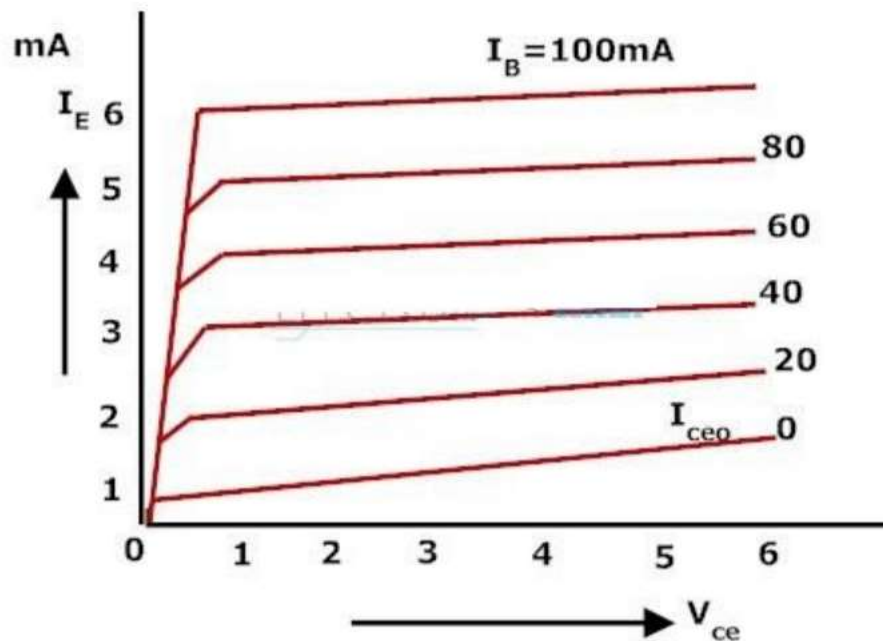


Output Characteristic



Procedure:

Input Characteristics:

1. Connect the circuit as per the circuit diagram.
2. Set $V_{CE} = 5V$, vary, V_{BE} in steps of $0.1V$ & note down the corresponding I_B and repeat the above procedure for $10V$ & so on.
3. Plot the graph: V_{CB} vs I_B for a constant V_{CE} .

Output Characteristics:

1. Connect the circuit as per the circuit diagram.
2. Set $I_B = 20\mu A$, vary V_{CE} in steps of $1V$ & note down the corresponding I_E . Repeat the above procedure for $40\mu A, 80\mu A$ & so on.
3. Plot the graph: V_{CE} vs I_C for a constant of I_B .

EXPERIMENT-9

Objective: To verify V-I characteristics of JFET.

Apparatus required

Power supply

Lab trainer kit

Jumper wires

Oscilloscope

Waveform generator

Multimeter

Theory

A JFET has three terminals as:

- 1) Source (S): The terminal through which the majority charge carriers enter the channel. Conventionally, the current entering at S is designated by I_S .
- 2) Drain (D): The terminal through which the majority charge carriers leave the channel. Conventionally, current entering the channel at D is designated by I_D . Drain-to-source voltage is V_{DS} .
- 3) Gate (G): the terminal that modulates the channel conductivity.

The JFET is a unipolar voltage controlled device. The drain current is controlled by the voltage applied at the gate. In the circuit shown self bias maintains drain current and mutual conductance g_m relatively constant. Constant g_m results a constant voltage gain. The reverse biased junction provides high input impedance.

JFET Parameters

1. Drain Resistance (r_d): It is given by the relation of small change in drain to source voltage (V_{DS}) to the corresponding change in Drain Current (I_D) for a constant gate to source voltage (V_{GS}), when the JFET is operating in pinch-off region.

$$r_d = \Delta V_{DS} / \Delta I_D \quad \text{at a constant } V_{GS} \text{ (from drain characteristics)}$$

2. Trans Conductance (g_m): Ratio of small change in drain current (I_D) to the corresponding change in gate to source voltage (V_{GS}) for a constant V_{DS} .

$$g_m = \Delta I_D / \Delta V_{GS} \quad \text{at constant } V_{DS} \text{ (from transfer characteristics).}$$

The value of g_m is expressed in mho's or Siemens (s).


3. Amplification factor (μ): It is given by the ratio of small change in drain to source voltage (V_{DS}) to the corresponding change in gate to source voltage (V_{GS}) for a constant drain current (I_D).

$$\mu = (\Delta V_{DS}/\Delta I_D) \times (\Delta I_D/\Delta V_{GS}) = \Delta V_{DS}/\Delta V_{GS}$$

ie. $\mu = r_d \times g_m$

FET Transfer Characteristics

FET Drain Characteristics

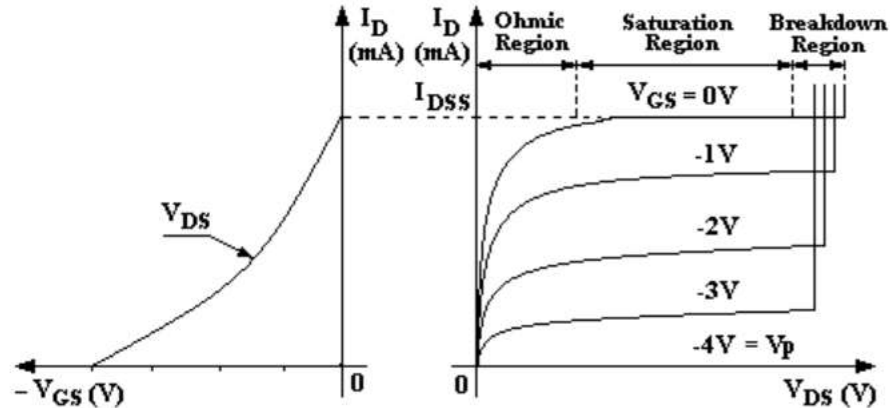

Procedure:

Drain Characteristics:

1. Connect the circuit as shown in the figure.
2. Keep $V_{GS} = 0V$ by varying V_{GG} .
3. Varying V_{DD} gradually in steps of 1V up to 10V note down drain current I_D and drain to source voltage (V_{DS}).
4. Repeat above procedure for $V_{GS} = -0.4, -0.8, -1.2$ and $-1.6 V$

Transfer Characteristics:

1. Connect the circuit as shown in the figure.
2. Set voltage $V_{DS} = 4V/8V$
3. Varying V_{DS} in steps of 0.5V until the current I_D reduces to minimum value.
4. Varying V_{GG} gradually, note down both drain current I_D and gate-source voltage (V_{GS}).
5. Repeat above procedure (step 3) for $V_{DS} = 4V/ 8V$