

Experiment No. 2

Objective: To determine unknown inductance using Hays bridge. of inductance by Hay's bridge **Apparatus Used:**

S. No.	Name of the apparatus	Quantity
1	Lab trainer kit	1
2	Multimeter	1
3	Unknown inductor	1

Theory: The Hay's Bridge differs from Maxwell's bridge by having resistor R1 in series with standard capacitor C1 instead of in parallel. It is immediately apparent that for large phase angles, R1 should have a very low value. The Hay's circuit is therefore more convenient for measuring high Q coils. The balance equations are again derived by substituting the values of the impedance of the bridge arms into the general equation for bridge balance. On separating real and imaginary terms, the balance equations are:

$$R_1 R_x + L_x / C_1 = R_2 R_3 \text{ ----- (1)}$$

$$R_x / \omega C_1 = \omega L_x R_1 \text{ ----- (2)}$$

Both equations 1 & 2 consist of L & R. By solving the above equations

$$R_x = \frac{\omega^2 C_1^2 R_2 R_3}{1 + \omega^2 C_1^2 R_1^2} \text{ ----- (3)}$$


$$L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 C_1^2 R_1^2} \text{ ----- (4)}$$

The expressions for the unknown inductance & resistance are consists of frequency term under balanced condition when two phase angles are equal, their tangents are also equal. Hence,


$$\tan\theta_L = \tan\theta_C \text{ (or) } Q = \frac{1}{\omega C_1 R_1} \text{ ----- (5)}$$

Substituting (5) in (4)

Circuit Diagram:

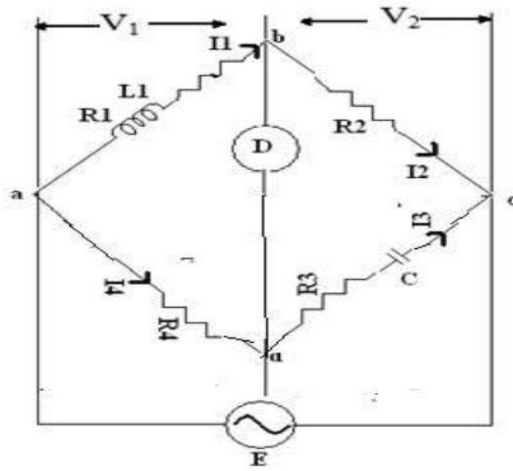

Phasor Diagram:

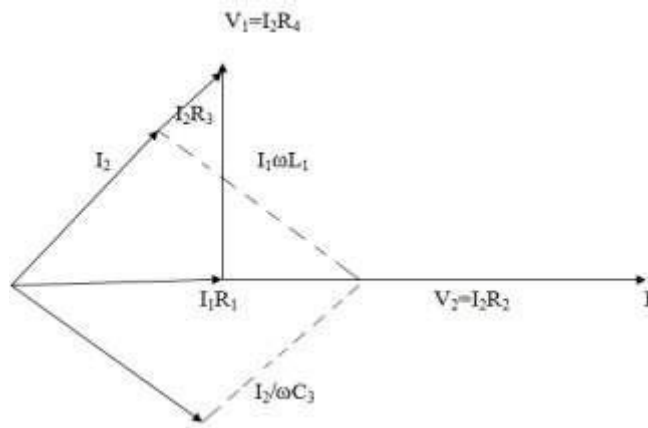

Procedure:

1. Switch ON the trainer & check the power supply.
2. Connect the unknown value of inductance (high Q) in arm marked L_x .
3. Vary R_2 for fine balance adjustment.
4. The balance of bridge can be observed by using head phone. Connect the output of the bridge at the input of the detector.
5. Connect the head phone at output of the detector, alternately adjust R_1 and proper selection of R_3 for a minimum sound in the head phone.
6. Finally disconnect the circuit and measure the value of R_1 at balance point using any multimeter. By substituting R_1 , R_3 and C_1 the unknown inductance can be obtained.

7. Observation Table:

S.No.	R_2 (K Ω)	R_3 (Ω)	C_1 (μ F)	L_x (mH)	L mH
1					
2					
3					

8. **Result:** After balancing the bridge, the values of R_1 , R_3 and C_1 are measured and found that the calculated value of L_x is almost equal to the actual value.