

### Experiment No.3

**Objective:** To determine unknown inductance by using Anderson's bridge

#### Apparatus Used:

S. No.	Name of the apparatus	Quantity
1	Lab trainer kit	1
2	Multimeter	1
3	Unknown inductor	1

**Theory:** In this bridge, the self inductance is measured in terms of a standard capacitor. This method is applicable for precise measurement of self-inductance over a very wide range of values. Figure below show the connections and the phasor diagram of the bridge for balanced conditions.

Let  $L_1$  = self inductance to be measured,  $R_1$  = resistance of self-inductor,  $r, R_2, R_3, R_4$  = known non-inductive resistance  $r_1$  = resistance connected in series with self-inductor,

At, balance,  $I_1 = I_3$  and  $I_2 = I_C + I_4$ .

Now,  $I_1 R_3 = I_C / j\omega C$  therefore,  $I_C = I_1 j\omega C R_3$ .


Writing the other balance equations.

$I_1 (r_1 + R_1 + j\omega L_1) = I_2 R_2 + I_C r$  and  $I_C (r_1 + j\omega C) = (I_2 - I_C) R_4$


By substituting  $I_C$  value and equating real and imaginary parts

$R_1 = R_2 R_3 / R_4 - r_1$

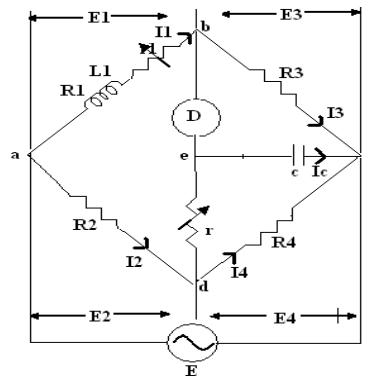$L_1 = C R_3 / R_4 \{ r_1 (R_4 + R_2) + R_2 R_4 \}$  **Circuit Diagram**



#### Phasor Diagram:

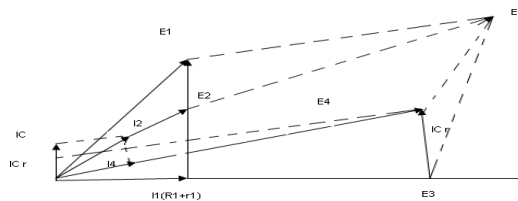

**Procedure:**

1. Connect the circuit as shown in the figure.
2. Connect the unknown inductance in L1.
3. Select any value of r.
4. Connect the multimeter between ground and output of imbalance amplifier.
5. Vary r1 and r, from minimum position, in clockwise direction.
6. Calculate the inductance L1 by substituting known values.

**Observation Table:**

S. No.	Actual value of L in mH	R in ohms	Practical value of L in mH

**Results:** The unknown inductance is determined using the Anderson's bridge.