

Experiment No. 5

ASTABLE MULTIVIBRATORS USING OP AMP

Aim: To design and setup symmetrical and asymmetrical astable multivibrators using Op-amp 741, plot the waveforms and measure the frequency of oscillation

Objectives: After completion of this experiment, student will be able to design and setup an astable multivibrators circuit using OP AMP.

Equipments/Components:

Sl. No	Name and Specification	Quantity required
1	Dual power supply +/- 15V	1
2	Function generator (0- 1MHz)	1
3	Oscilloscope	1
4	Bread board	1
5	IC 741C	1
6	Resistor	5
7	Capacitor 0.1 μ F	1
8	Diode 1N4001	2
9	Probes and connecting wires	As required.

Theory:


In this circuit, the opamp is operated in saturation mode and the output swings between $+V_{sat}$ and $-V_{sat}$ giving square wave output. This circuit is also called free running oscillator or square wave generator. A positive feedback with feedback factor $\beta = R_1 / (R_1 + R_2)$ is provided to the non-inverting terminal. When $V_o = +V_{sat}$, the capacitor C starts to charge to $+V_{sat}$ through R. when the capacitor voltage crosses $+\beta V_{sat}$, output switches from $+V_{sat}$ to $-V_{sat}$. Now the voltage appearing at the non-inverting terminal is $-\beta V_{sat}$ and capacitor discharges through R towards $-V_{sat}$. When the capacitor voltage crosses $-\beta V_{sat}$, the output switches from $-V_{sat}$ to $+V_{sat}$ and this process continues to generate square wave output with time period $T = T_{on} + T_{off} = 2RC \ln[(1+\beta)/(1-\beta)]$. In asymmetrical astable multivibrators, the charging and discharging time of capacitor is made unequal to get asymmetrical square wave with different T_{on} and T_{off} .

Procedure:

1. Check the components.
2. Setup the symmetric astable multivibrator circuit on the breadboard and check the connections.
3. Switch on the power supply.
4. Observe output and capacitor voltage on two channels of the oscilloscope simultaneously.
5. Draw the waveforms on the graph.
6. Measure the frequency of oscillation and duty cycle.
7. Repeat the procedures for asymmetric astable multivibrator.

a) SYMMETRICAL ASTABLE MULTIVIBRATOR

Circuit Diagram:

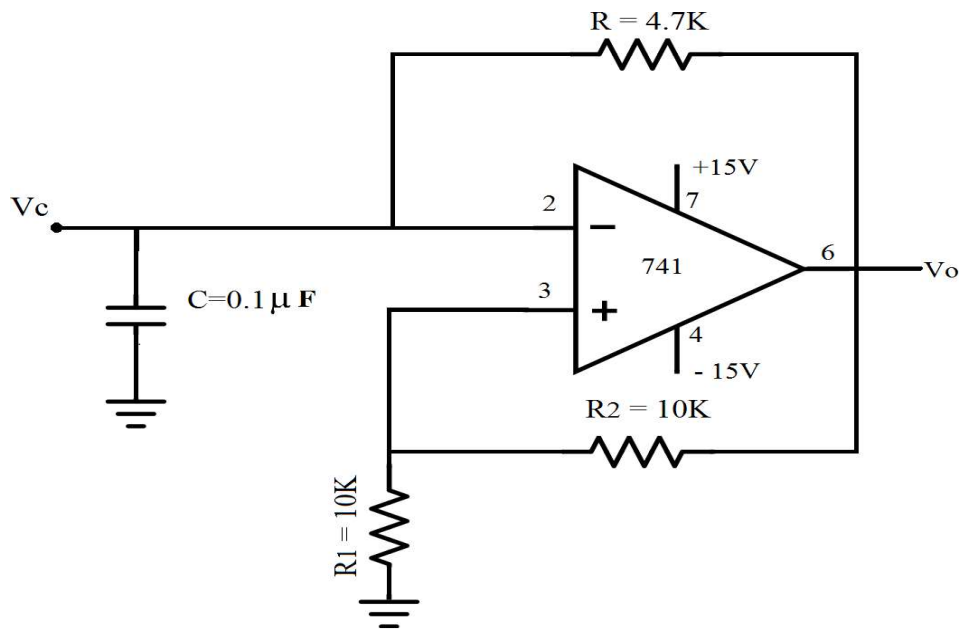

SYMMETRICAL ASTABLE MULTIVIBRATOR

Design:

Given $f = 1 \text{ KHz}$

So $T = 1/f = 1\text{ms}$

And $\beta = R_1 / (R_1 + R_2)$

Let $R_1 = 10\text{K}\Omega$, and $R_2 = 10\text{K}\Omega$


Then $\beta = 0.5$

Therefore $T = 2.2RC$

Let $C = 0.1\mu\text{F}$ Then $R =$
 $4.7\text{K}\Omega$

b) ASYMMETRICAL ASTABLE MULTIVIBRATOR

Circuit Diagram:

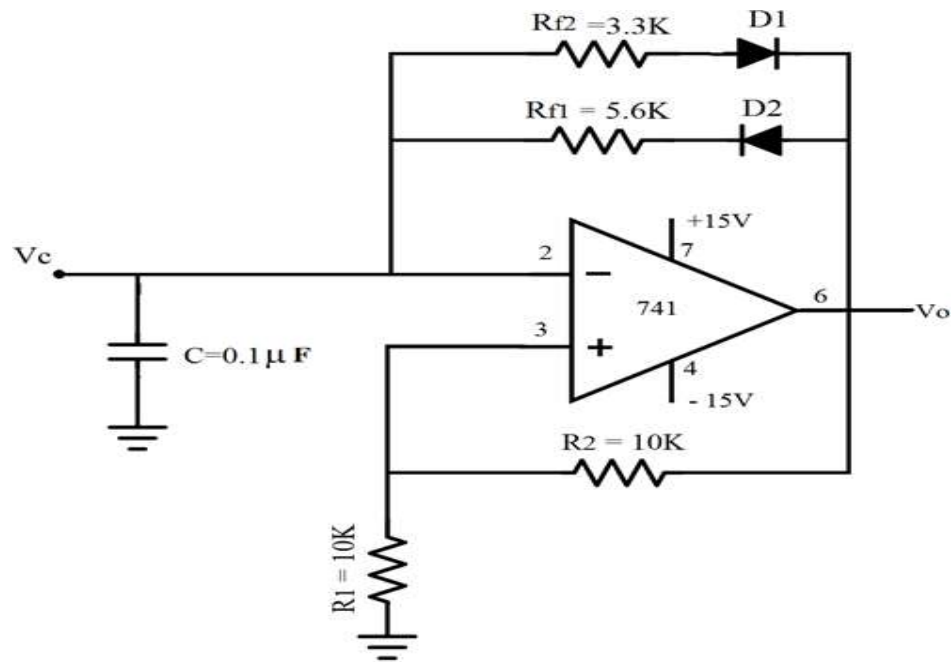

ASYMMETRICAL ASTABLE MULTIVIBRATOR

Design:

Given $f = 1 \text{ KHz}$

So $T = T_{\text{on}} + T_{\text{off}} = 1/f = 1 \text{ ms}$

Also Duty cycle $= T_{\text{on}}/(T_{\text{on}}+T_{\text{off}}) = 0.66$ or 66% Solving above two equations, $T_{\text{on}} = 0.66 \text{ ms}$ $T_{\text{off}} = 0.33 \text{ ms}$

For $\beta=0.5$,

$$T_{\text{on}} = 1.1R_{f1}C = 0.66 \text{ ms}$$

$$\text{Let } C = 0.1 \mu\text{F}$$

$$\text{Then } R_{f1} = 6.2 \text{ K}\Omega = 5.6 \text{ K}\Omega \text{ (Std)}$$

$$\text{Similarly } T_{\text{off}} = 1.1R_{f2}C = 0.33 \text{ ms}$$

$$\text{Then } R_{f2} = 3 \text{ K}\Omega = 3.3 \text{ K}\Omega \text{ (Std)}$$

bservation:

a) Symmetrical astable multivibrators

$$V_o(p-p) = ?$$

$$f = ?$$

$$\text{Duty cycle} = ?$$

b) Asymmetrical astable multivibrators

$$V_o(p-p) = ?$$

$$f = ?$$

$$\text{Duty cycle} = ?$$

Graph:

a) Symmetrical astable multivibrators

b) Asymmetrical astable multivibrators

Result:

MONOSTABLE MULTIVIBRATOR USING OP AMP

Aim: To design and setup a monostable multivibrator using Op-amp 741 and

- (i) Plot the waveforms (ii) Measure the time delay

Objectives: After completion of this experiment the students are able to design and set up the monostable multivibrator circuit and delay circuits.

Equipments/Components

Sl. No.	Name and spification	Quantity
1	Dual Power Supply +/-15V	1
2	Resistors	4
3	Capacitor 0.1 μ F;0.01 μ F	1 each
4	IC μ A 741	1
5	Function generator (0-1)MHz	1
6.	Oscilloscope	1
7.	Diode 1N 4001	2
8	Bread board	1
9	Connecting wires and probes	As required

Theory:

The monostable multivibrator is also called as one shot multivibrator. The circuit produces a single pulse of specified duration in response to each external trigger pulse. It always has one stable state (+V_{sat}). When an external trigger is applied, the output state changes and the new state is called quasi stable state (-V_{sat}). The circuit remains in this state for a fixed interval of time and then it returns to the original state after this interval. This time interval is determined discharging of the capacitor from 0.7V to - β V_{sat}.The time period of quasi stable state or the delay is given by


$$T = 0.69RC$$

Procedure:

1. Check the components.
2. Setup the monostable multivibrator circuit on the breadboard and check the connections.
3. Switch on the power supply.

4. Put the function generator output to square wave mode. Adjust the amplitude to 5V.
5. Observe trigger input , output and capacitor voltage on different channels of the oscilloscope simultaneously.
6. Draw the waveforms on the graph.
7. Measure the time delay .

Circuit Diagram:

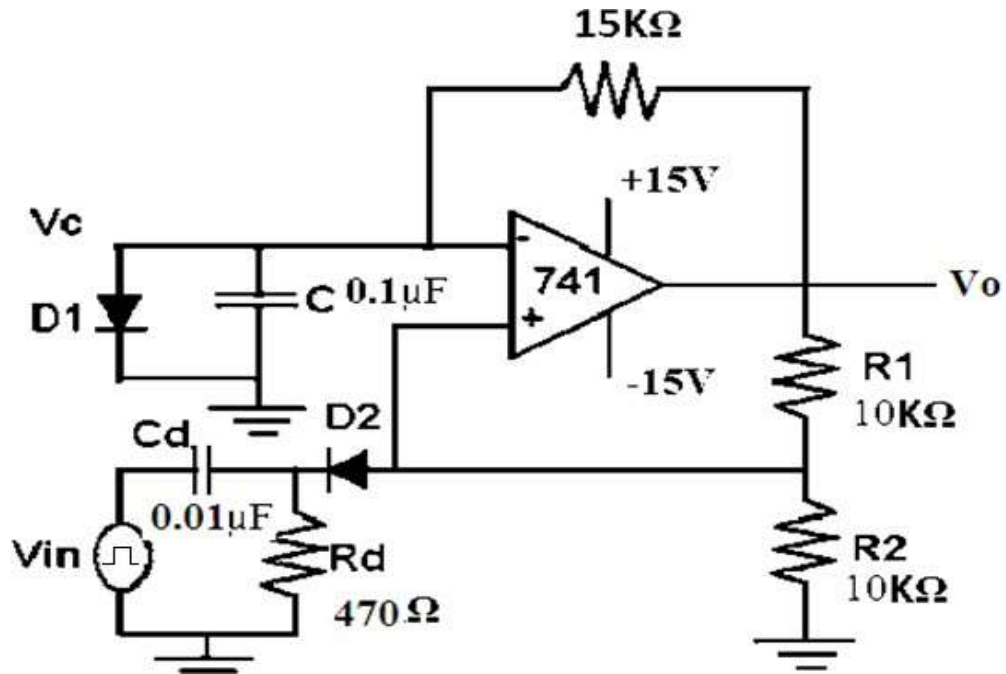

Design:

$$\text{Time Period } T = 0.69RC$$

$$\text{Let } T = 1\text{ms}; \text{ and } C = 0.1\mu\text{F}.$$

$$\text{Then } R = 15\text{K}\Omega \text{ Feedback factor}$$

$$\beta = R_2 / (R_1 + R_2) \text{ Let } \beta = 0.5 \text{ or } 1/2$$

$$R_2 / (R_1 + R_2) = 1/2$$

$$\text{If } R_1 = 10\text{K}\Omega ; R_2 = 10\text{K}\Omega$$

For triggering circuit

$$R_d C_d = 0.0016t$$

Let $t = 3\text{ms}$ and $C_d = 0.01 \mu\text{F}$; then $R_d =$
 470Ω D_1 & D_2 are diodes 1N 4001

Observations:

Measured time period or delay =?

Graph:

Result: