

Experiment No.6

SCHMITT TRIGGER

Aim: To design and setup a Schmitt trigger, plot the input output waveforms and measure V_{UT} and V_{LT} .

Objectives: After completion of this experiment, student will be able to design and setup a Schmitt trigger circuit using OP AMP.

Equipments/Components:

Sl .No	Name and Specification	Quantity required
1	Dual power supply +/- 15V	1
2	Function generator(0- 1MHz)	1
3	Oscilloscope	1
4	Bread board	1
5	IC 741C	1
6	Resistor	3
7	Probes and connecting wires	As required.

Theory:


It is a regenerative comparator or it is a comparator with hysteresis. This circuit uses positive feedback and the op-amp is operated in saturation. The output can take two values

$+V_{sat}$ and $-V_{sat}$. When output = $+V_{sat}$, the voltage appearing at the non-inverting terminal is V_{UT} or $UTP = +V_{sat}(R_1/R_1+R_2)$ called the upper threshold point. Similarly When output = $-V_{sat}$, the voltage appearing at the non-inverting terminal is V_{LT} or $LTP = -V_{sat}(R_1/R_1+R_2)$ called the lower threshold point. When V_{in} is greater than UTP, the output will switch from $+V_{sat}$ to $-V_{sat}$. Similarly When V_{in} is less than LTP; the output will switch from $-V_{sat}$ to $+V_{sat}$ which is shown in the graph. The difference between UTP-LTP is called hysteresis. Hysteresis avoids false triggering of the circuit by noise. Hysteresis curve is the plot of V_o versus V_{in} . Schmitt trigger circuit is used to convert any irregular wave into square wave.

Procedure:

1. Check the components.
2. Setup the circuit on the breadboard and check the connections.
3. Switch on the power supply.
4. Give $V_i = 10 \text{ V}_{pp} / 1\text{KHz}$ sine wave.
5. Observe input and output on two channels of oscilloscope simultaneously.
6. Note down and draw the input and output waveforms on the graph.

Circuit Diagram

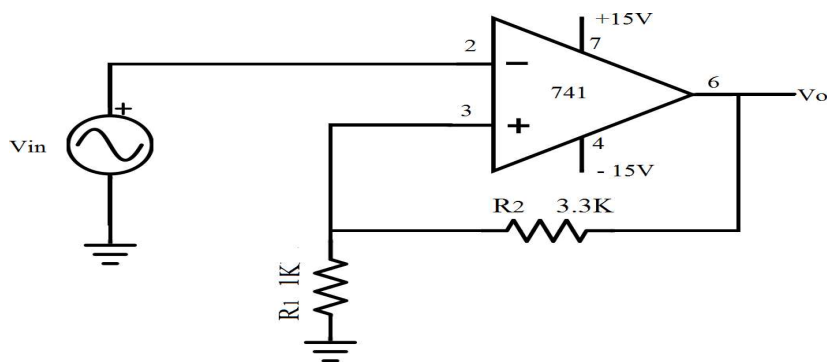

Design:

$$UTP = +V_{sat} \left(\frac{R_1}{R_1 + R_2} \right)$$

Let $UTP = +3\text{V}$ and $LTP = -3\text{V}$,

$$V_{sat} = +13\text{V}$$

$$UTP, +3 = +13 \left(\frac{R_1}{R_1 + R_2} \right)$$

Let $R_1 = 1 \text{ K}\Omega$

Then $R_2 = 3.3 \text{ K}\Omega$

Observations:

UTP =

LTP =

Graph:

Result: