

## Experiment no. 7

**AIM:** To design, construct and plot the frequency response of second order low pass having the  $f_c$  of 1 kHz.

### APPARATUS REQUIRED:

S.No.	Name of the Apparatus	Range/Value	Qty
1.	Bread Board	-	1
2.	IC Power Supply	$\pm 15$ V	1
3.	Resistor	10 k $\Omega$ , 5.86 k $\Omega$ 1.6 k $\Omega$	1 2
4.	IC 741 Op-Amp	-	1
5.	CRO	20 MHz.	1
6.	Function Generator	0-3MHz.	1
7.	Capacitor	0.1 $\mu$ F	2
8.	Connecting Wires	-	Few

### THEORY:

An improved filter response can be obtained by using a second order active filter. A second order filter consist of two RC pairs has a roll-off rate of  $-40$ db/decade. The transfer function of a Low pass filter is  $H(s)$ . For  $n=2$ , the damping factor  $\alpha = 1.414$ , the pass band gain  $A_0 = 3 - \alpha = 1.586$ . Cutoff frequency of the filter  $= 1/2\pi RC = f_c$ . HPF is the complement of the Lowpass filter and can be obtained simply by interchanging R and C in the low pass configuration

### DESIGN:


$$f_c = 1\text{KHz, Assume } C = 0.1\mu\text{F, } R = 1/2\pi f_c C =$$

The gain for the second order filter is known as 1.5816.

$$\text{Let } R_i = 10\text{K}\Omega, \text{ Gain} = A_0 = 1.5816 \Rightarrow 1 + R_f / R_i = 1.586 \Rightarrow R_f = 0.586$$

**CIRCUIT DIAGRAM:**

**Low Pass Filter**

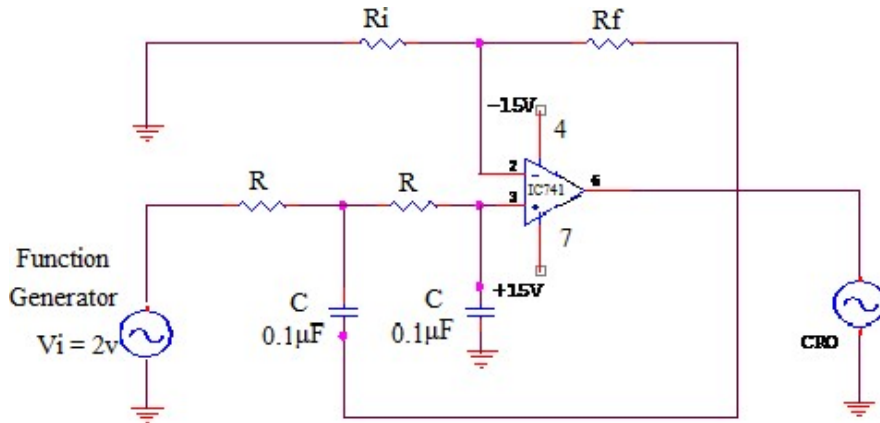

**PROCEDURE:**

1. Connect the Low pass filter circuit as shown in the circuit diagram.
2. Give an input signal  $V_i$  of 2V(p-p) and measure the output voltage for different frequency from the CRO.
3. Plot the frequency response  $20 \log V_o/V_i$  versus input frequency and find 3db frequency.
4. Determine the cut-off frequency from the plot.

**TABULATION:**

**Low Pass Filter**

**INPUT VOLTAGE:  $V_i =$  volts**

Frequency Hz	Output voltage $V_o$ volts	Gain in db $20 \log V_o/V_i$

**Result -**