

Experiment no. 8

AIM: To design, construct and plot the frequency response of second order High pass filter having the f_c of 1 kHz.

APPARATUS REQUIRED:

S.No.	Name of the Apparatus	Range/Value	Qty
1.	Bread Board	-	1
2.	IC Power Supply	± 15 V	1
3.	Resistor	10 k Ω , 5.86 k Ω 1.6 k Ω	1 2
4.	IC 741 Op-Amp	-	1
5.	CRO	20 MHz.	1
6.	Function Generator	0-3MHz.	1
7.	Capacitor	0.1 μ F	2
8.	Connecting Wires	-	Few

THEORY:

An improved filter response can be obtained by using a second order active filter. A second order filter consist of two RC pairs has a roll-off rate of -40 db/decade. The transfer function of a Low pass filter is $H(s)$. For $n=2$, the damping factor $\alpha = 1.414$, the pass band gain $A_0 = 3 - \alpha = 1.586$. Cutoff frequency of the filter $= 1/2\pi RC = f_c$. HPF is the complement of the Lowpass filter and can be obtained simply by interchanging R and C in the low pass configuration

DESIGN:

$$f_c = 1\text{KHz, Assume } C = 0.1\mu\text{F, } R = 1/2\pi f_c C =$$

The gain for the second order filter is known as 1.5816.

$$\text{Let } R_i = 10\text{K}\Omega, \text{ Gain} = A_0 = 1.5816 \Rightarrow 1 + R_f / R_i = 1.586 \Rightarrow R_f = 0.586 R_i =$$

Second order High Pass Filter:



